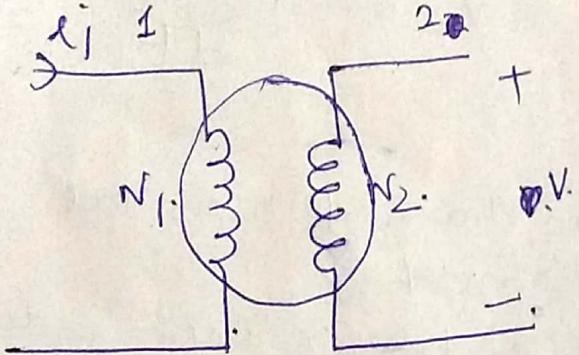


## Dot Convention in Magnetically Coupled Ckts



Whenever the current is flowing in one coil, it induces a voltage in the nearby coil.

When the current flows through one coil, it is the other coil.


flux of the one coil gets coupled with the other coil. This kind of ckt's are magnetically coupled ckt's.

The voltage induced in the nearby coil is given by

$$V = M \frac{di}{dt}$$

M is the mutual inductance b/w the two coils:

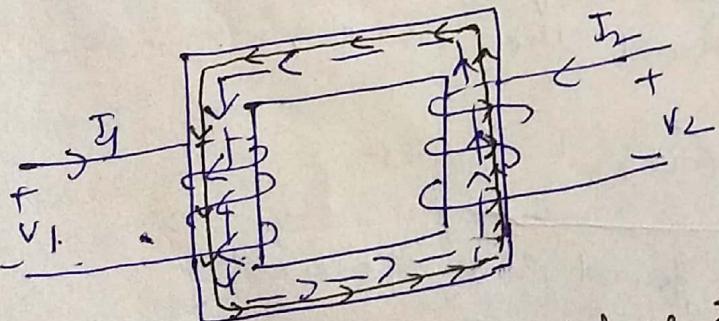The polarity of the induced voltage depends on the way the windings are wound around the core.



$$V_{21} = M \frac{di_1}{dt}$$

voltage induced in 2 due to current flowing in 1.

$$V_{12} = M \frac{di_2}{dt}$$

These two fluxes are adding to each other. The current  $I_1$  &  $I_2$  are flowing simultaneously.


The voltage which will be generated due to mutual coupling will be the:

$$V_1 = L_1 \frac{di}{dt} + M \frac{di_2}{dt}$$

$$V_2 = L_2 \frac{di_2}{dt} + M \frac{di_1}{dt}$$

Self induced emf

Emf induced due to mutual coupling

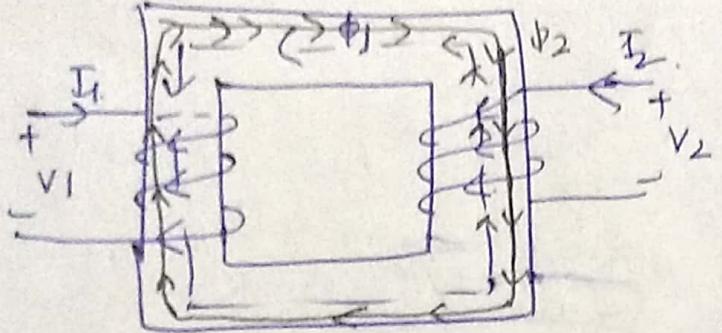

$$V_{21} = -m \frac{di_1}{dt}$$

$$V_{12} = -m \frac{di_2}{dt}$$

If the number of turns of winding has changed then the direction of flux has been changed. The net flux will be opposite and hence the induced voltage in the coil due to mutual coupling will be negative.

$$V_1 = L_1 \frac{di_1}{dt} - m \frac{di_2}{dt}$$

$$V_2 = L_2 \frac{di_2}{dt} - m \frac{di_1}{dt}$$

Hence the polarity of the induced voltage depends on the ~~direction of the~~ way in which the windings are wound around the core.

This is a lengthy process

Everything we have to find the polarity of the voltage we have to see the direction of the windings & the direction of the flux.

This is very lengthy process


We put dots on the either side of the coil & we put the dot on all the coils which are coupled together.

Depending on the co-wraps which are entering


or leaving the dot, we determine the polarity of the induced voltage due to mutual coupling.
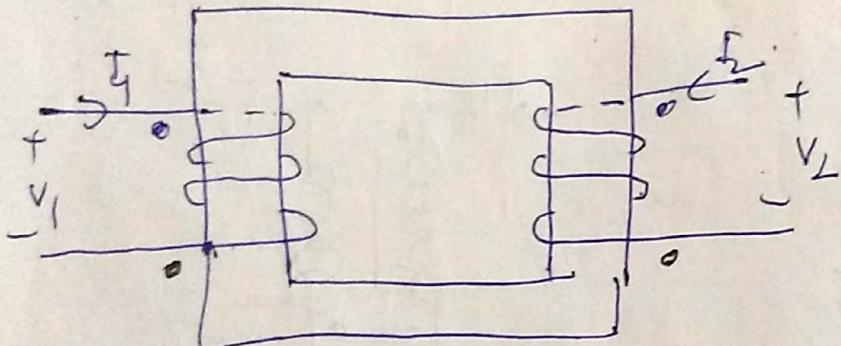
### Dot Convention



If two currents are entering (leaving) the dot at the same time then voltage generated due to mutual inductance will be positive



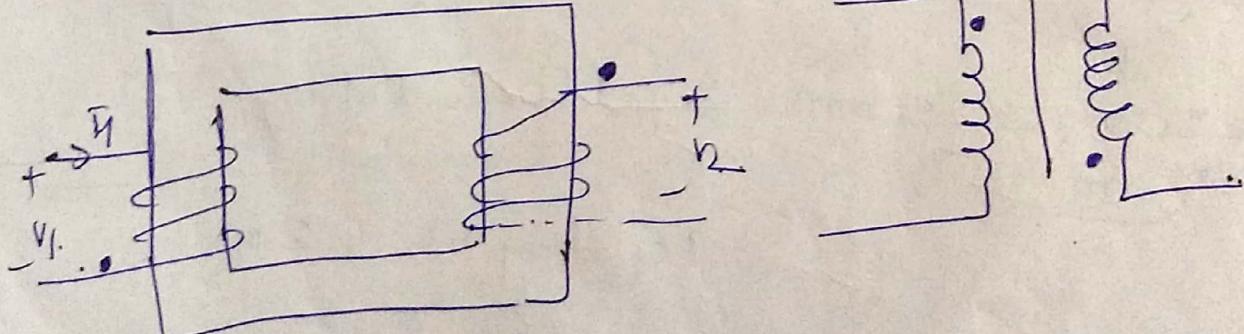If one current is entering (leaving) the dot and another current is leaving (entering) the dot then voltage generated due to mutual inductance will be negative.




Dot Convention

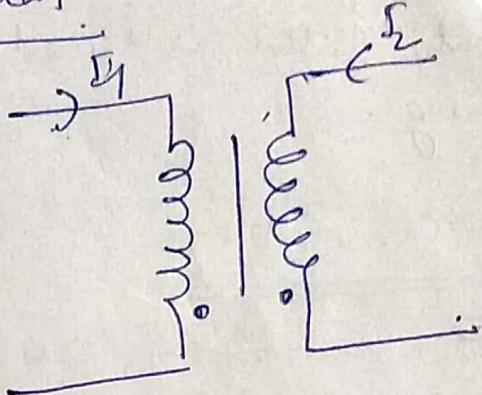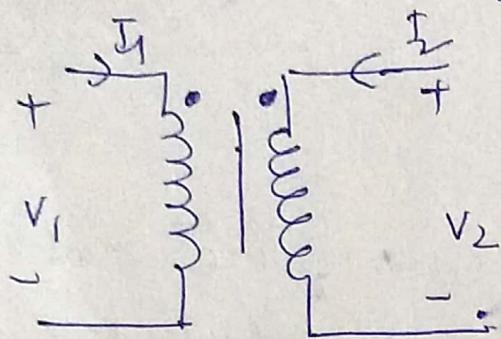


$$V_1 = L_1 \frac{di_1}{dt} + M \frac{di_2}{dt}$$
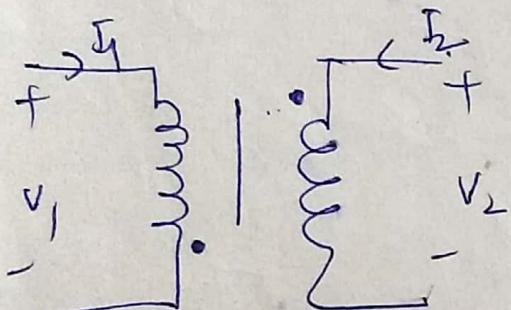
$$V_2 = L_2 \frac{di_2}{dt} + M \frac{di_1}{dt}$$



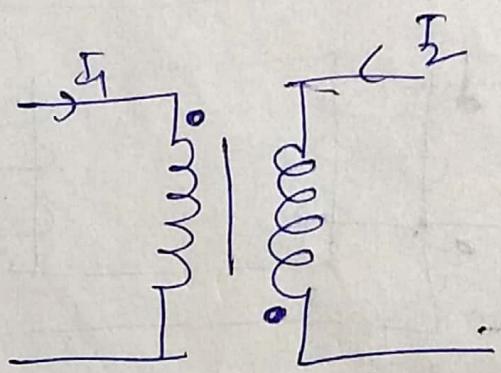
$$V_1 = L_1 \frac{di_1}{dt} - M \frac{di_2}{dt}$$




$$V_2 = L_2 \frac{di_2}{dt} - M \frac{di_1}{dt}$$

### Coupled Coils in Series

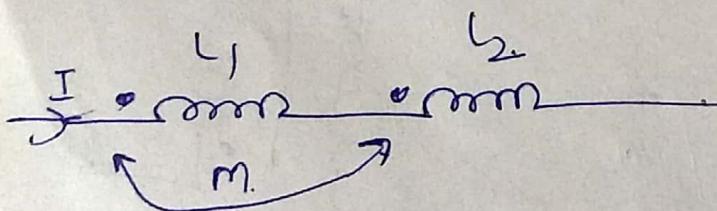


Series aiding  
connection

$$L_{eq} = L_1 + L_2 + 2M$$

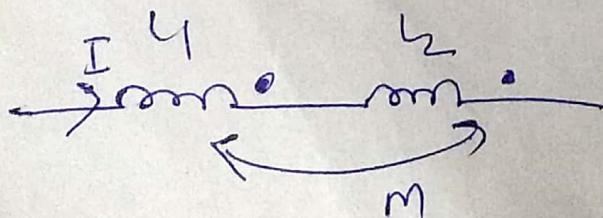

$$L_{eq} = L_1 + L_2 - 2M$$

Series aiding.

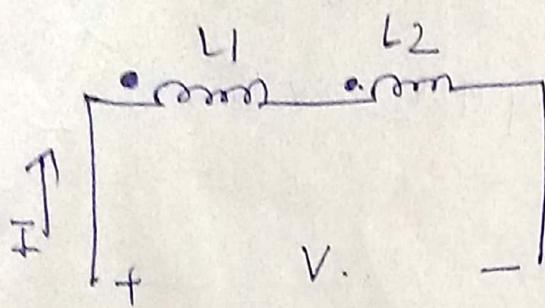


$$V = j\omega L_1 I + j\omega L_2 I + j\omega M I + j\omega M I$$

$$\frac{V}{I} = Z_{eq}$$


$$j\omega [L_1 + L_2 + 2M] = Z_{eq}$$

$$\boxed{Z_{eq} = L_1 + L_2 + 2M}$$

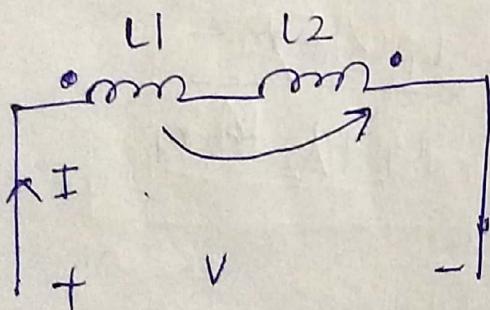


$$V = j\omega L_1 I + j\omega L_2 I - j\omega M I - j\omega M I$$

$$\boxed{V = L_1 + L_2 - 2M}$$

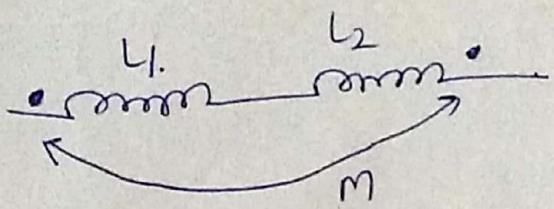


Series opposing connection

$$L = L_1 + L_2 - 2M$$

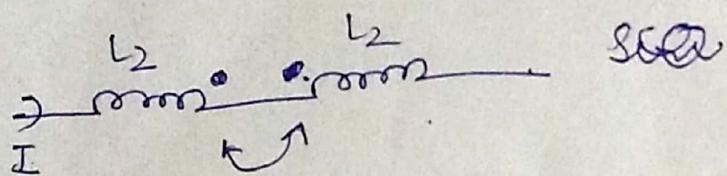


Series


### Coupled Coils in Parallel

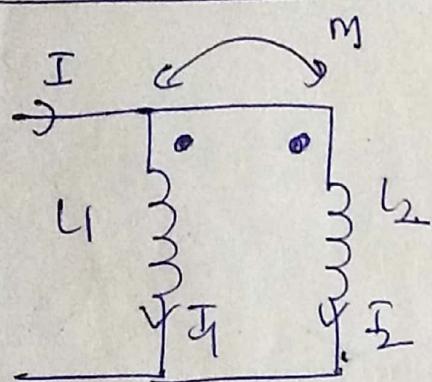
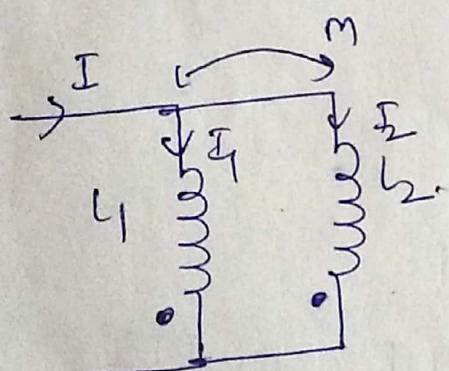
$$L_{eq} = \frac{L_1 L_2 - M^2}{L_1 + L_2 - 2M}$$


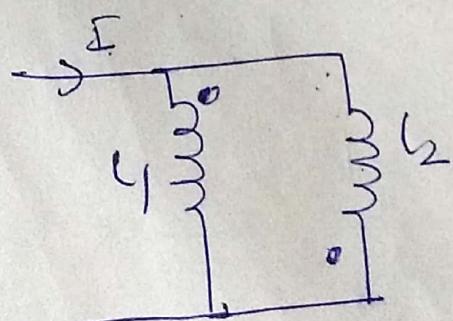
$$L_{eq} = \frac{L_1 L_2 + M^2}{L_1 + L_2 + 2M}$$




$$L_{eq} = \frac{L_1 L_2 + M^2}{L_1 + L_2 + 2M}$$

Effect cause

$M_{21}$  = Effect on 2 due to current flowing in 1.

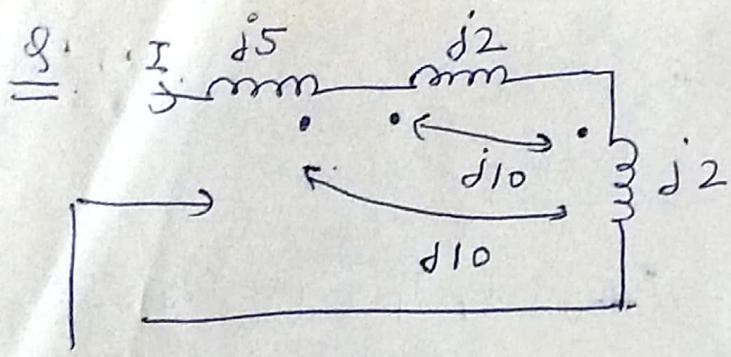$M_{12}$  = Effect on 1 due to current flowing in 2.



2.


$$V = j\omega L_1 I + j\omega L_2 I + j\omega L_3 I - j\omega M_{21} I +$$
 ~~$+ j\omega M_{31} I - j\omega M_{12} I + j\omega M_{32} I$~~ 
 ~~$- j\omega M_{13} I + j\omega M_{23} I$~~ 
 $= j5 + j2 + j2 - j10 - j10 - j10 + j10$

$$V = j\omega L_1 I + j\omega L_2 I + j\omega L_3 I - j\omega M_{31} I$$
 $+ j\omega M_{32} I - j\omega M_{13} I + j\omega M_{23} I$ 


↓ effect cause  
on 1 due to 3

$$V = j^9 I$$

$$\boxed{\frac{V}{I} = j^9}$$

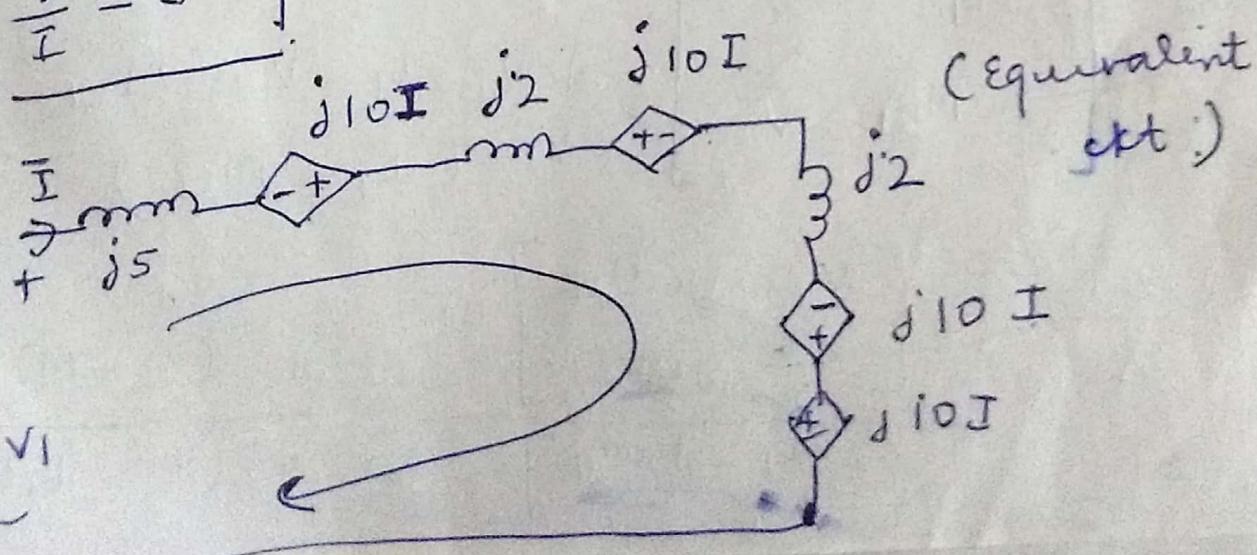

## Coupled Coils in Parallel.

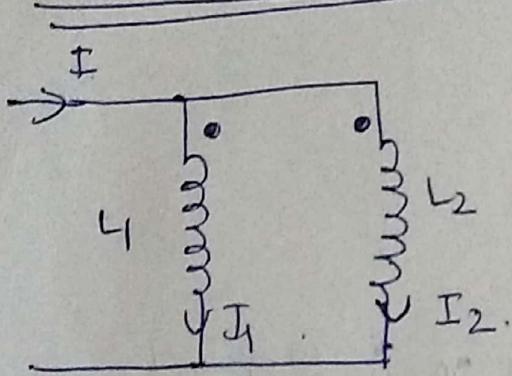

$$\underline{\text{In KVL } 1}$$

$$-V + j\omega L_1 I_1 + j\omega M_{12} I_2 = 0$$

$$\underline{\text{In KVL } 2}$$

$$-V + j\omega L_2 I_2 + j\omega M_{21} I_1 = 0$$

$$\begin{bmatrix} V \\ V \end{bmatrix} = \begin{bmatrix} j\omega L_1 & j\omega M_{12} \\ j\omega M_{21} & j\omega L_2 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$

$$\Delta = \begin{bmatrix} j\omega L_1 & j\omega M_{12} \\ j\omega M_{21} & j\omega L_2 \end{bmatrix} = j^2 \omega^2 L_1 L_2 - j^2 \omega^2 M^2 = j^2 \omega^2 (L_1 L_2 - M^2)$$

$$\Delta_1 = \begin{bmatrix} V & j\omega M_{12} \\ V & j\omega L_2 \end{bmatrix} \Rightarrow V(j\omega L_2) - V(j\omega M_{12}) = V j\omega (L_2 - M_{12})$$

$$\Delta_2 = \begin{bmatrix} j\omega L_1 & V \\ j\omega M_{21} & V \end{bmatrix} \Rightarrow V j\omega L_1 - V j\omega M_{21} = V j\omega (L_1 - M_{21})$$

$$I_1 = \frac{\Delta_1}{\Delta} = \frac{\begin{bmatrix} V & j\omega M_{12} \\ V & j\omega L_2 \end{bmatrix}}{\begin{bmatrix} j\omega L_1 & j\omega M_{12} \\ j\omega M_{21} & j\omega L_2 \end{bmatrix}} = \frac{j\omega (L_2 - M) V}{\omega^2 (M^2 - L_1 L_2)}$$


$$\frac{I_2}{I} = \frac{\begin{bmatrix} j\omega L_1 & V \\ j\omega M & V \end{bmatrix}}{\begin{bmatrix} j\omega L_1 & j\omega M \\ j\omega M & j\omega L_2 \end{bmatrix}} = \frac{j\omega(L_1 - M)V}{\omega^2(M^2 - L_1L_2)}$$

$$I = I_1 + I_2$$

$$= \frac{j\omega(L_1 + L_2 - 2M)V}{\omega^2(M^2 - L_1L_2)}$$

$$Z = \frac{V}{I} = j\omega \left( \frac{L_1L_2 - M^2}{L_1 + L_2 - 2M} \right)$$

$$\boxed{L_{eq} = \frac{L_1L_2 - M^2}{L_1 + L_2 - 2M}}$$

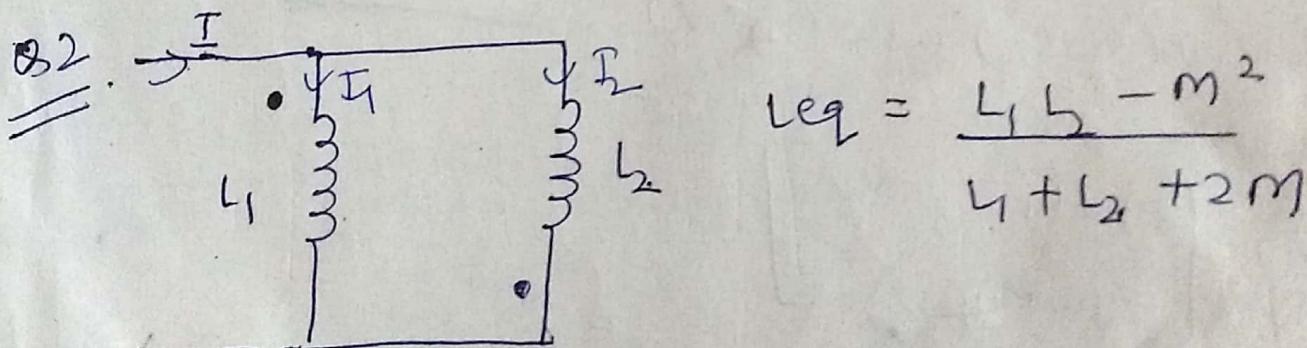

KVL 1

$$-V_1 + j\omega L_1 I_1 - j\omega M_{12} I_2 = 0 \quad \text{--- (1)}$$

KVL 2

$$-V_1 + j\omega L_2 I_2 - j\omega M_{21} I_1 = 0 \quad \text{--- (2)}$$

$$\begin{bmatrix} v \\ v \end{bmatrix} = \begin{bmatrix} j\omega L_1 & -j\omega M_{12} \\ -j\omega M_{21} & j\omega L_2 \end{bmatrix} \begin{bmatrix} I \\ I \end{bmatrix}$$

$$\Delta = \begin{bmatrix} j\omega L_1 & -j\omega M_{12} \\ -j\omega M_{21} & j\omega L_2 \end{bmatrix}$$

$$\begin{aligned} \Delta &= j\omega L_1 (j\omega L_2) - (j\omega M_{21})(j\omega M_{12}) \\ &= j^2 \omega^2 L_1 L_2 - j^2 \omega^2 M^2 \\ \Delta &= \underline{j^2 \omega^2 (L_1 L_2 - M^2)} \end{aligned}$$

$$D_1 = \begin{bmatrix} v & -j\omega M_{12} \\ v & j\omega L_2 \end{bmatrix}$$

$$D_1 = v(j\omega L_2) + j\omega M_{12}(v)$$

$$D_2 = \begin{bmatrix} j\omega L_1 & v \\ -j\omega M_{21} & v \end{bmatrix}$$

$$D_2 = v(j\omega L_1) + v(j\omega M_{21})$$

$$I_1 = \frac{D_1}{\Delta} = \frac{v(j\omega L_2) + j\omega M_{12}(v)}{j^2 \omega^2 (L_1 L_2 - M^2)} = \frac{v j \omega (L_2 + M)}{\omega (M^2 - L_1 L_2)}$$

$$I_1 = \frac{v(L_2 + M)}{j\omega (L_1 L_2 - M^2)}$$

$$Z_1 = \frac{V_1 i_2 (L_2 + M)}{\omega_2 (M_2 - L_2)}$$

$$I \boxed{j\omega \left( \frac{L_2 - M^2}{L_2 + M} \right) = \frac{V}{I}}$$

$$I_2 = \frac{D_2}{\Delta} = \frac{\begin{bmatrix} j\omega L_1 & V \\ -j\omega M_{21} & V \end{bmatrix}}{\begin{bmatrix} j\omega L_1 & -j\omega M_{12} \\ -j\omega M_{21} & j\omega L_2 \end{bmatrix}}$$

$$I_2 = \frac{V(j\omega L_1) + V(j\omega M_{21})}{j^2 \omega^2 (L_2 - M^2)}$$

$$I_2 = \frac{V j \omega (L_1 + M_{21})}{j^2 \omega^2 (L_1 L_2 - M^2)} = \frac{j \omega (L_1 + M) V}{\omega^2 (M^2 - L_1 L_2)}$$

$$I = I_1 + I_2$$


$$= \frac{V(L_2 + M)}{j\omega(L_1 L_2 - M^2)} + \frac{V(L_1 + M)}{j\omega(L_1 L_2 - M^2)}$$

$$I = \frac{V(L_1 + L_2 + 2M)}{j\omega(L_1 L_2 - M^2)}$$

$$j\omega \left( \frac{L_1 L_2 - M^2}{L_1 + L_2 + 2M} \right) = \frac{V}{I}$$


$$\boxed{\text{leg} = \frac{L_1 L_2 - M^2}{L_1 + L_2 + 2M}}$$

The Equivalent Inductance leg of the ct.

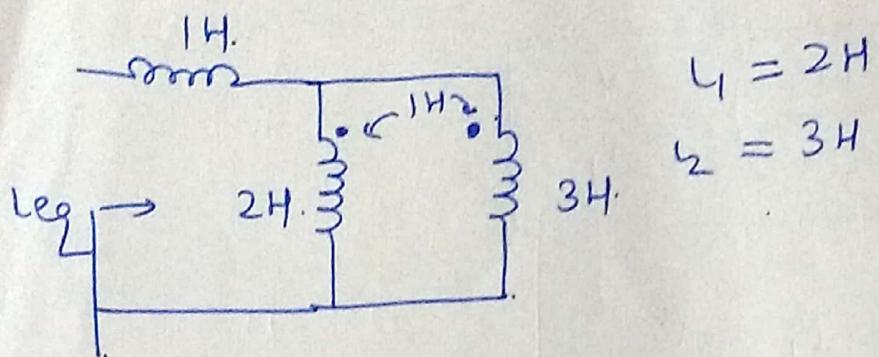


$$L_0 = \frac{L_1 L_2 - m^2}{L_1 + L_2 - 2m} = \frac{2 \times 3 - (1)^2}{2 + 3 - 2} = \frac{5}{3} H$$
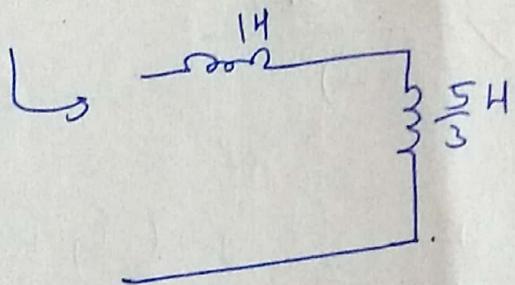
$$L_{eq} = L + L_0 = 1 + \frac{5}{3} = \frac{8}{3} H$$



If no magnetic coupling

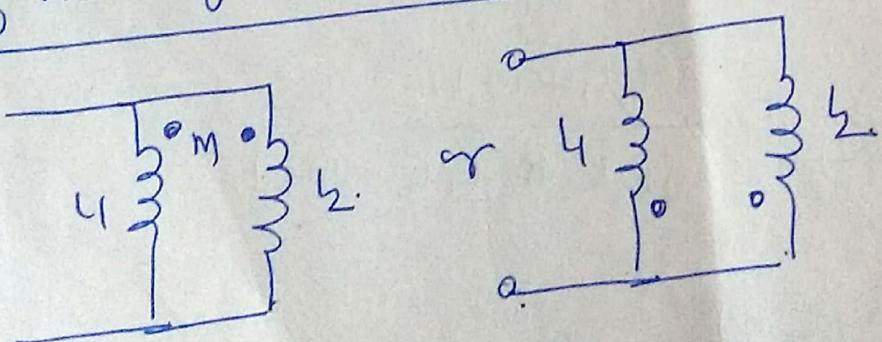

$$L_{eq} = \frac{L_1 L_2 - m^2}{L_1 + L_2 - 2m}$$

If no magnetic coupling

$$L_{eq} = \frac{L_1 L_2}{L_1 + L_2}$$


$$\therefore L_{eq} = \frac{1}{L_1} + \frac{1}{L_2}$$

$$L_1 = L_2 + L_3 = 10 \text{ H}$$

$$m_{12} = m_{21} = 1 \text{ H}$$

$$m_{13} = m_{31} = 2 \text{ H}$$

$$m_{23} = m_{32} = 3 \text{ H}$$

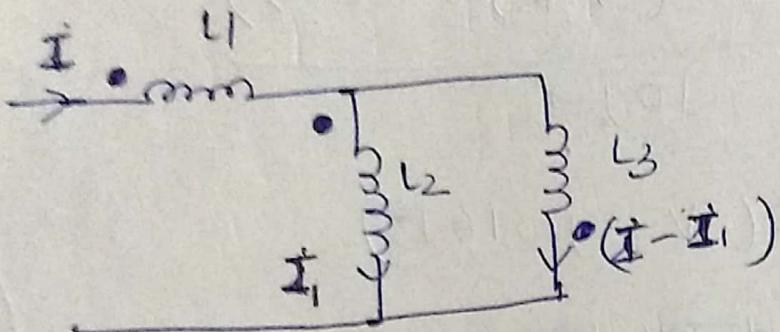

$$V = \frac{j\omega L_1 I + j\omega L_2 I + j\omega M_{12} I_1 - j\omega M_{13} (I - I_1)}{j\omega M_{21} I - j\omega M_{23} (I - I_1)} \quad (1)$$

$$V = j\omega (L_1 + M_{21} - M_{23} - M_{13}) I + j\omega (L_2 + M_{12} + M_{13} + M_{23}) I_1$$

$$V = j\omega (10 + 1 + 2 + 3) I + j\omega (10 + 1 + 2 + 3) I_1$$

$$V = j\omega (11 - 5) I + j\omega (16) I_1$$

$$V = 6j\omega I + 16j\omega I_1 \quad (1)$$

$$\begin{aligned} \text{KVL 2} \\ = & -V_1 + j\omega L_1 I + j\omega L_3 (I - I_1) + j\omega M_{12} I_1 \\ & - j\omega M_{13} (I - I_1) - j\omega M_{31} I - j\omega M_{32} I_1 = 0 \\ & -V + j\omega I (L_1 + L_3 - M_{13} - M_{31}) \\ & - j\omega (L_3 - M_{13} - M_{12} + M_{32}) I_1 = 0 \end{aligned}$$

$$-\overset{+}{V}_1 + j\omega I (10 + 10 - 2 - 2) - j\omega \underline{I} (10) = 0 \text{ [v]} \\ \boxed{V = -10j\omega I + j\omega I (16)} \quad (2)$$

$$V = j\omega 6I \cancel{+ j\omega 16(V \cancel{- j\omega I(16)})} \\ \underline{10j\omega}$$

$$V = j\omega 6I \cancel{+ 1.6(V - j\omega 16I)}$$

$$2.6V = j\omega 6I \cancel{- V} + j\omega 25.6I$$

$$2.6V = 31.6 \underline{I}$$

$$\boxed{\frac{V}{I} = 12.5 \Omega}$$

$$= j\omega (12.5) \\ \underline{P_{L_{eq}}}$$