


Three phase system

①

Application of alternating current was limited to heating & lighting lamps in early days. Years later A.C. motors were developed that was operated on A.C. and its performance was analysed. In A.C. motors, Induction motor was not self starting and required two windings. This developed the need for requirement of more than one phase system. Moreover the power generation and its transmission over long distances demanded higher voltage levels and justified the use of 3 phase a.c..

Generation of 3 phase emfs

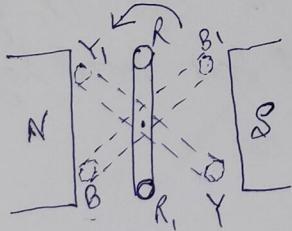Suppose there are three coils namely RR₁, YY₁, BB₁ rotating anticlockwise at a uniform speed in magnetic field due to poles N.S.




This arrangement is similar to single phase emf generation where only one coil was present. Here we have three coils placed at 120° to each other.



Shot on OnePlus

By KULDEEP

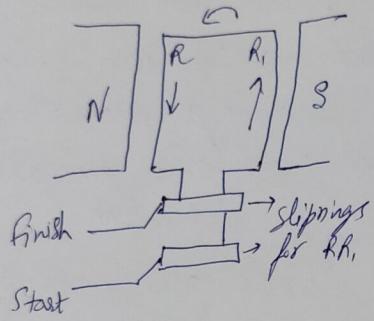Generator of 3 phase voltage is based on Faraday's law of electromagnetic induction. When the loop $R R_1$ has moved through 90° to the position as shown, the generated emf in the coil is at its maximum value and its direction round the loop is from 'start' to ~~opp.~~ 'finish' as shown.



Similarly the loop YY_1 has emf generated on the same lines as the loop are rotated in same manner, has exactly same amplitude as that generated in RR_1 , but lags by 120° . In the same manner, the coil BB_1 has same amplitude of emf generation but it lags YY_1 by 120° . Thus from RR_1 phase it has total lage of 240° .



Shot on OnePlus

By KULDEEP



(2)

If the Instantaneous value of emf generated in phase RR_1 is represented by $e_R = E_m \sin \theta$, then instantaneous value in YY_1 is represented by

$$e_Y = E_m \sin(\theta - 120^\circ)$$

and in BB_1 is

$$e_B = E_m \sin(\theta - 240^\circ)$$

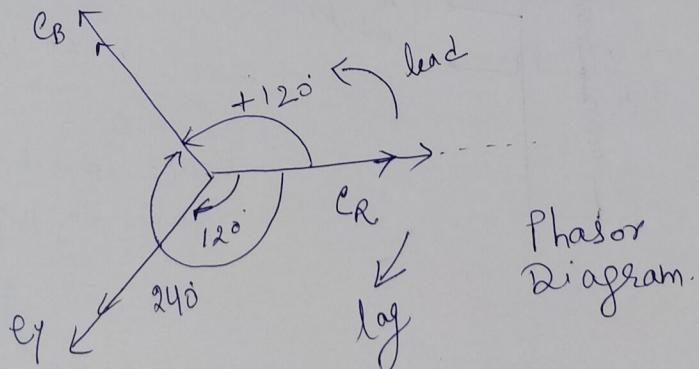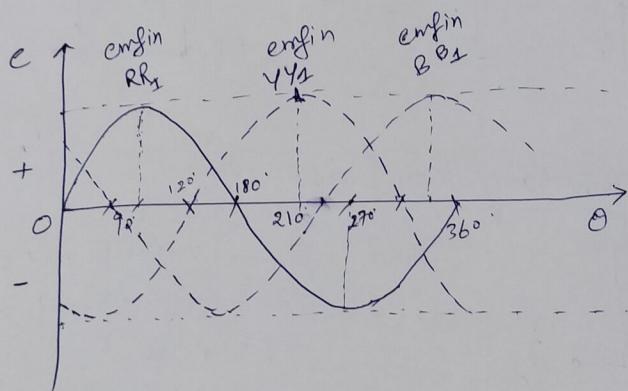


Phasor Diagram.




Shot on OnePlus

By KULDEEP

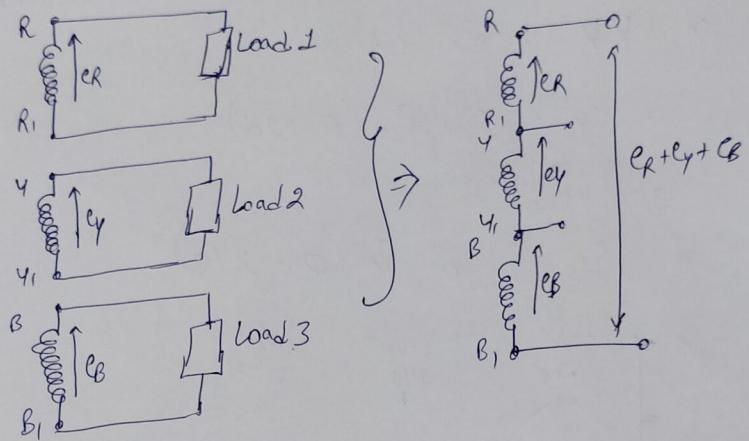Delta Connection and star connection of three phase winding, their line to phase quantity relation.



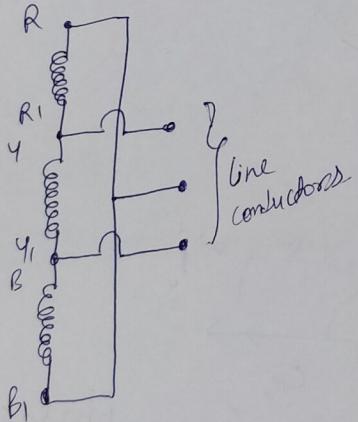→ Delta Connection of three phase winding.



At instantaneous value of
delta emf from B to R is

$$e_R + e_Y + e_B$$

$$= E_m \{ \sin\theta + \sin(\theta - 120^\circ) + \sin(\theta - 240^\circ) \}$$

$$= E_m \left(\frac{1}{2} \sin\theta - \frac{1}{2} \sin\theta - 0.866 \cos\theta - \frac{1}{2} \sin\theta + 0.866 \cos\theta \right)$$

$$= 0$$


Hence conductor R & B are joined together




Shot on OnePlus

By KULDEEP

(3)

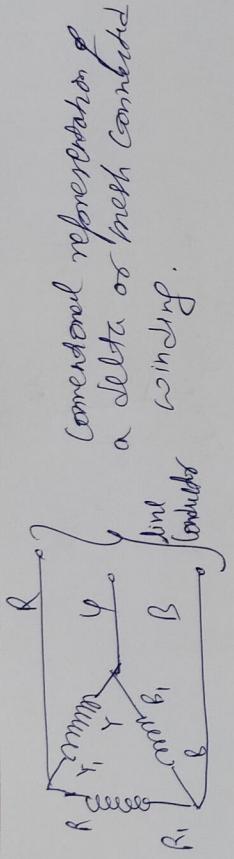

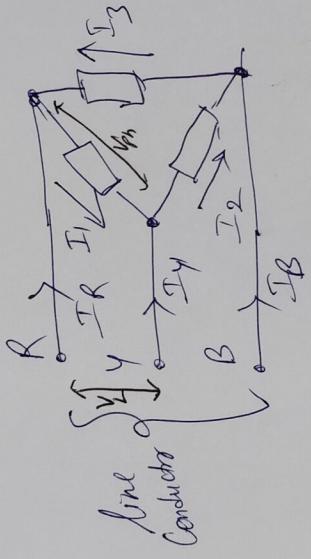
Consider. Delta connected generator with winding connections as given above & has three line conductors and this is connected to load. Now the load can be in Star or Delta form. Let us consider Delta connected load.



Here. we have three phase load which is combination of three single phase load and it is connected in Delta form. The current in the line conductors is line current I_A , I_B and I_C . The current in the loads as depicted by I_1 , I_2 and I_3 are rms value of phase current. Since the load is balanced, these currents are equal in magnitude and differs by 120° .



Shot on OnePlus
By KULDEEP

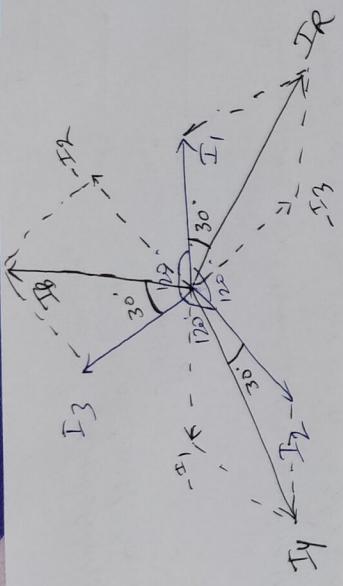

$$\text{As } \bar{I}_R + \bar{I}_3 = \bar{I}_1$$

$$\Rightarrow \bar{I}_R = \bar{I}_1 - \bar{I}_3.$$

Similarly

$$\bar{I}_Y + \bar{I}_1 = \bar{I}_2$$

$$\bar{I}_Y = \bar{I}_2 - \bar{I}_1$$

$$\text{and also } \bar{I}_B = \bar{I}_3 - \bar{I}_2.$$

As $\bar{I}_R = 2\bar{I}_1 \cos 30^\circ$
Since magnitude of \bar{I}_1, \bar{I}_2 and \bar{I}_3 are equal
as imbalanced load,

$$\Rightarrow \bar{I}_R = \sqrt{3}\bar{I}_1$$



$$\text{or } \boxed{\bar{I}_L = \sqrt{3} \bar{I}_{ph}}$$

Line current is $\sqrt{3}$ times the phase current.

It is seen from Delta Connection of load that the
line and phase voltages are same i.e.
 $\boxed{V_L = V_{ph}}$



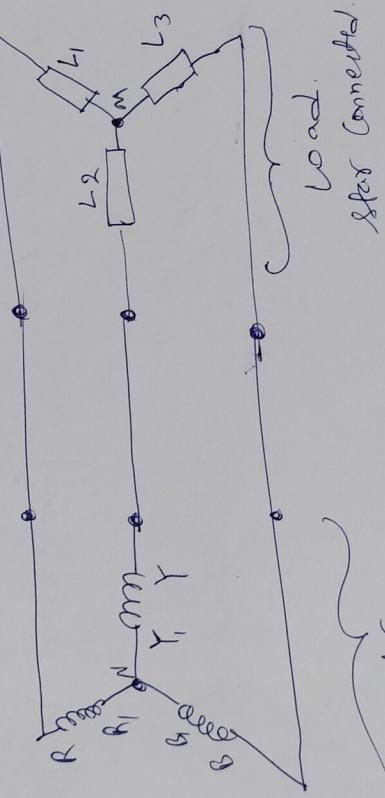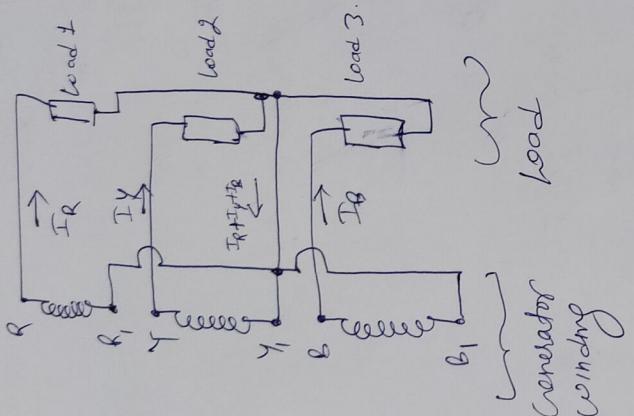
(4) Star Connection and line to phase quantity of three phase windings.



Three wire star connected system.



Shot on OnePlus
By KULDEEP

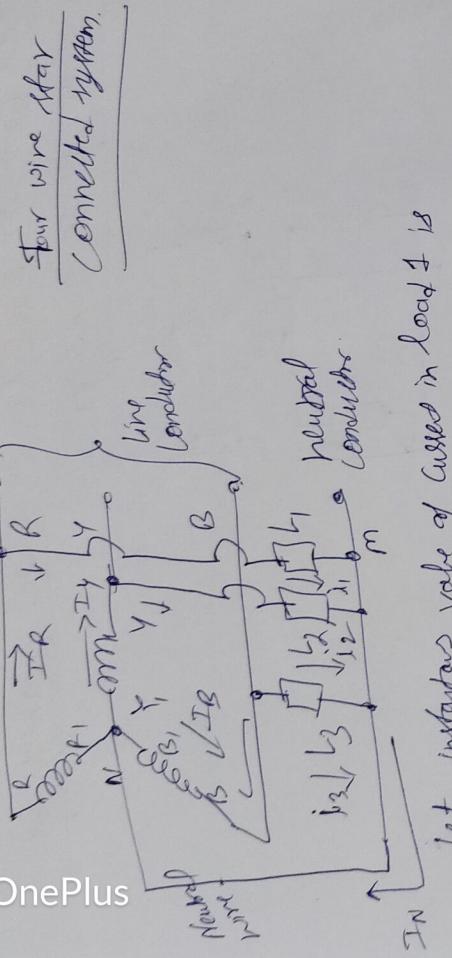

Let instantaneous value of current in load 1 is
 $i_1 = I_m \sin \theta$, then
 $i_2 = I_m \sin(\theta - 120^\circ)$
 $i_3 = I_m \sin(\theta - 240^\circ)$


The instantaneous value of resultant current in neutral conductor is given by
 $I_N = i_1 + i_2 + i_3 = I_m \{ \sin \theta + \sin(\theta - 120^\circ) + \sin(\theta - 240^\circ) \}$

$$I_N = I_m \times 0$$


$$\bar{I}_N = 0$$



15

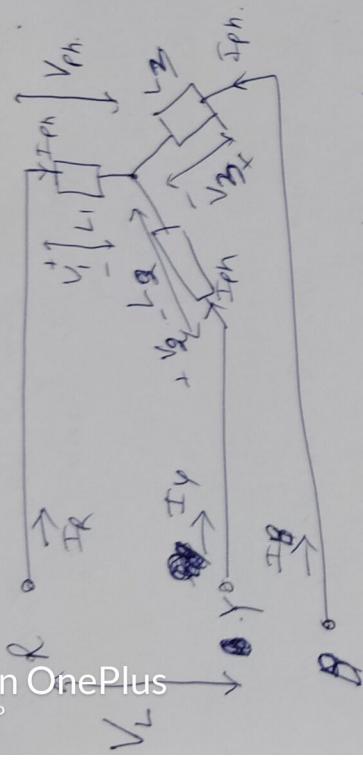

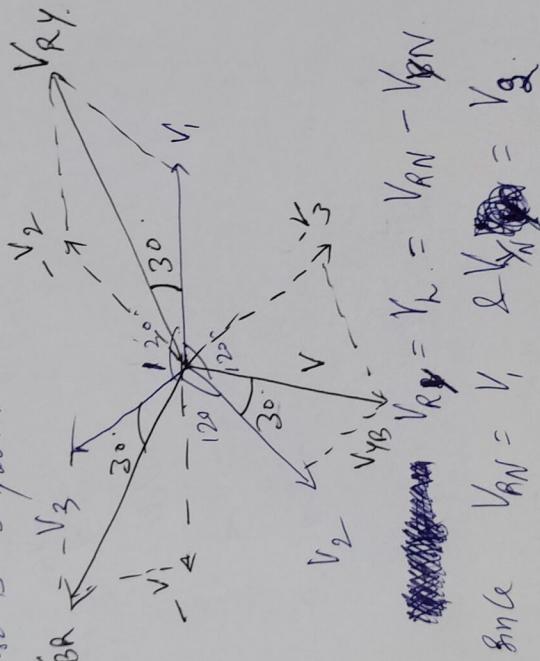Let the phase voltages in different phases be V_1 , V_2 and V_3 . Since balanced loads there, the phasor is as follows



28

$$V_{RN} = V_R - V_N$$

$$V_{\text{out}} = V_i \cdot \frac{R_2}{R_1 + R_2} = V_{\text{og}}$$

$$V_{R4} = V_L = 2 V_1 \log_{30}$$

Since magnitude of V_1 , V_2 and V_3 are equal in balanced load,

$$V_L = \sqrt{3} V_{ph} \quad \text{or} \quad V_R Y = \sqrt{3} V_Y$$

It is seen from star connection of load that the line and phase currents are same i.e.,

$$I_L = I_{Ph}$$

Ex In a three phase balanced star connected load, supply voltage is 208 V. Each load has a resistance of 35 Ω determine the power factor, total power and phase & line currents of the system.

Sol Supply voltage = 208 V

$$V_L = 208 V$$

$$V_{Ph} = 208 / \sqrt{3} = 120 \text{ Volt}$$

Current in each phase is calculated as

$$\vec{I}_a = \frac{120 \angle 0^\circ}{35} = 3.428 \angle 0^\circ$$

$$\vec{I}_b = \frac{120 \angle -120^\circ}{35} = 3.428 \angle -120^\circ$$

$$\vec{I}_c = \frac{120 \angle -240^\circ}{35} = 3.428 \angle -240^\circ$$

load is resistive hence reactive power is $\vec{I}^2 R$.
 \Rightarrow Total power = $3 \vec{I}^2 R = 3 \times (3.428)^2 \times 35$
 $= 3 \times 411.3 \text{ Watts}$

Also $I_L = I_{Ph}$. Since it is star connection.
P.F. is unity since resistive load.


Q) The phase sequence of the star connected generator is ABC.

Find the phase angles θ_1 and θ_2 .

Find the magnitude of line voltages.

Find the line currents.

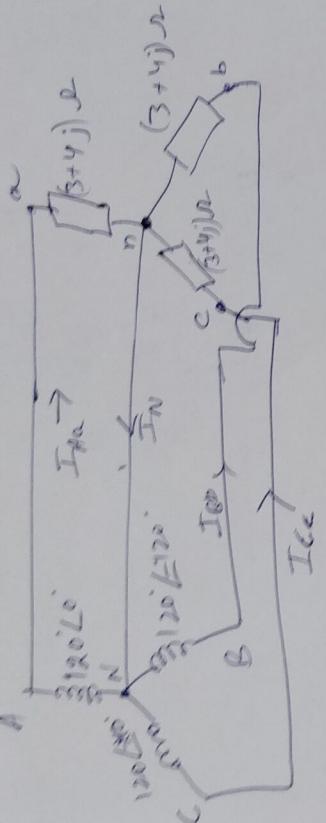Ans: $\theta_1 = -120^\circ$, $\theta_2 = 240^\circ$, $I_{L1} = I_{L2} = I_{L3} = 0$.



$$\text{Ans: } \theta_1 = -120^\circ, \theta_2 = 240^\circ$$

$$\text{Q) } E_L = \sqrt{3} E_n = 120^\circ \angle 0^\circ \times \sqrt{3} = 208 \text{ V.}$$

$$\text{Q) } V_{an} = 120^\circ \angle 0^\circ$$

$$V_{bn} = 120^\circ \angle 120^\circ$$

$$V_{cn} = 120^\circ \angle -120^\circ$$

$$I_{an} = I_{pn} = \frac{V_{an}}{Z_{an}} = \frac{120^\circ \angle 0^\circ}{3+4j} = \frac{120^\circ \angle 0^\circ}{\sqrt{5} \angle 53.13^\circ}$$

$$I_{bn} = 24 \angle -53.13^\circ$$

$$I_{cn} = \frac{120^\circ \angle -120^\circ}{\sqrt{5} \angle 53.13^\circ} = 24 \angle -173.13^\circ$$

$$T_{an} = \frac{120^{\circ} - 24^{\circ}}{57.5516} = 24 \angle 66.87$$

$$T_N = T_{\theta_9} + T_{\theta_6} + T_{c_c}$$

$$t = \frac{h_0}{g} \sqrt{\frac{2}{\pi}}$$

