

ELECTRICAL ENGINEERING

ASSIGNMENT-5

MAGNETIC CIRCUITS.

HARDIK KALRA

AS

DTU/2K16/AS/834

Ans-1

$$\frac{di}{dt} = \frac{12}{0.01} = 1200 \text{ A/s.}$$

$$M = \mu_0 \frac{N_1 N_2 A}{l}$$

$$e = N \frac{d\phi}{dt} = 1000 \times \frac{\phi}{t} = 1000 \frac{6 \times 0.05}{0 \times 0.01}$$

1.2 mV

$$M = \frac{\mu_0 \phi}{2} = 1000 \times \frac{60}{100} \times 0.05 \times 10^{-3} = 6 \times 10^{-3} \text{ H} \\ = 6 \text{ mH}$$

$$e = 6 \times 10^{-3} \left(\frac{12}{0.01} \right) = 7.2 \text{ V}$$

$$L = \frac{N \phi}{i} = 1000 \frac{6 \times 0.05 \times 10^{-3}}{5} = 10^{-2} \text{ H} = 10 \text{ mH.}$$

Ans-2

$$N_1 = 1500, l_1 = 60 \text{ cm}$$

$$N_2 = 500, A = 20 \times 10^{-4} \text{ m}^2$$

$$(a) M = \frac{\mu_0 N_1 N_2 A}{l} = \frac{4\pi \times 10^{-7} \times 1500 \times 500 \times 20 \times 10^{-4}}{60 \times 10^{-2}} \\ = 3.14 \text{ mH.}$$

$$(b) \quad \dot{e} = 3.14 \times 10^{-3} \times 250 \\ = 0.75 \text{ V}$$

Ans - 3

$$N_1 = 50, \quad N_2 = 505, \quad A = 2 \times 10^{-4} \\ l = 12 \text{ cm}, \quad I = 0.2 \text{ A}, \quad v = 5000,$$

$$M = \frac{4\pi \times 10^{-7} \times 50 \times 505 \times 2 \times 10^{-4}}{5 \times 2 \times 10^{-2}} = 52.8 \text{ mH}$$

$$C = M \frac{di}{dt} = 52.8 \times 10^{-6} \times 0.2 \times 5000 \\ = 0.0528 \text{ V}$$

Ans - 4

$$N = 1000, \quad l = 100 \text{ cm} = 1 \text{ m}$$

$$l_1 = l_2, \quad N_1 = N_2$$

$$d_1 = 3 \text{ cm}, \quad d_2 = 6 \text{ cm}$$

$$M_1 = \frac{\mu N_1 N_2 A_1}{l_1}, \quad M_2 = \frac{\mu N_1 N_2 A_2}{l_2}$$

$$M_1 = \frac{4\pi \times 10^{-7} \times 10^4 \times \pi \times 9 \times 10^{-4}}{4 \times 100 \times 10^{-2}} = 0.888 \text{ mH}$$

$$M_2 = \frac{4\pi \times 10^{-7} \times 10^4 \times \pi \times 36 \times 10^{-4}}{4 \times 100 \times 10^{-2}} = 3.55 \text{ mH}$$

$$u = \frac{\mu_0 N^2 A l}{L_1} \\ = \frac{4\pi \times 10^{-7} \times 10^6 \times \pi \times 9 \times 10^{-4}}{4} = 0.888 \text{ mH}$$

$$l_{12} = 3.55 \text{ mH}$$

$$K = \frac{M}{\sqrt{L_1 L_2}} = \frac{0.888}{\sqrt{0.888 \times 3.55}} = 0.5$$

Ans - 5

$$N_1 = 12000, I_1 = 5A, \phi_1 = 0.05 \text{ mWb}$$

$$N_2 = 15000, I_2 = 5A, \phi_2 = 0.075 \text{ mWb}$$

$$(a) M = \frac{N \phi}{i}$$

$$M_{12} = \frac{N_2 \phi_{12}}{i}$$

$$(b) T_{12} = R_1 + \frac{R_2}{K} = \frac{15000 \times (45 \times 0.05)}{5} = 0.0675 \text{ H.}$$

As

- 4.5% of flux produced

by 1 link current.

$$M_{12} = 0.0675 = 67.5 \text{ mH}$$

$$K = \frac{M}{\sqrt{L_1 L_2}}$$

$$L_1 = \frac{N_1 \phi_1}{I_1} = \frac{12000 \times 0.05 \times 10^{-3}}{5} = 0.12 \text{ H}$$

$$L_2 = \frac{N_2 \phi_2}{I_2} = \frac{15000 \times 0.075 \times 10^{-3}}{5} = 0.225$$

$$\sqrt{0.12 \times 0.225}$$

Ans - 6

$$N_2 = 600$$

$$N_1 = 30$$

$$A = 100 \times 10^{-4} \text{ m}^2 = 10^{-2} \text{ m}^2$$

$$l = 150 \times 10^{-2} \text{ m} = 1.5 \text{ m}$$

$$(a) M = \frac{\mu N_1 N_2 A}{l} = \mu_0 \mu_r \frac{N_1 N_2 A}{l} = \frac{4\pi \times 10^{-7} \times 2000 \times 30 \times 6}{\frac{150 \times 10^{-2}}{5}}$$

$$= \frac{4\pi}{5} \times 10^{-12} \times 10^{-2}$$

$$= 0.302 \text{ H.}$$

$$(b) e = \frac{M di}{dt} = 0.302 \times \frac{10}{10^{-2}} = 302 \text{ V}$$

Ans - 7

$$(i) \frac{V_1}{V_2} = \frac{13.8}{11.5} = \frac{6}{5}$$

$$\frac{P_i}{P} = 1 - \frac{1}{n} = 1 - \frac{5}{6} = \frac{1}{6}$$

$$P = 6 P_i = 600 \text{ kVA.}$$

(ii)

$$\frac{V_1}{V_2} = \frac{13.8}{2.3} = 6$$

$$\frac{P_i}{P} = 1 - \frac{1}{6} = \frac{5}{6}$$

$$\Rightarrow P = \frac{6}{5} P_i$$

$$= \frac{6}{5} \times 100 = 120 \text{ kVA}$$

Ans-8 $N_1 = 90$ $R_1 = 0.067 \Omega$
 $N_2 = 100$ $R_2 = 0.232 \Omega$

(a) $R_i = n^2 R_1$

$$n = \frac{N_2}{N_1} = 2$$

$$R_i = 4 \times 0.067$$

$$R_i = 0.268 \Omega$$

(b) $R_2' = \frac{R_2}{n^2} = \frac{0.232}{4} = 0.058 \Omega$

(c) Total $= R_1 + R_2' = 0.067 + 0.058$
 $= 0.125 \Omega$

Ans-9

Voltage applied $= \frac{1}{10}$ rated voltage $= 60 \text{ V}$

$$I_0 = 100 \text{ A}$$

$$P_{\text{input}} = 1.2 \text{ kW} = P_c$$

$$I_c = I_0^2 (R_1 + R_2)$$

$$R_1 + R_2 = \frac{1.2 \times 10^3}{10^4} = 0.12 \Omega$$

$$X_1 + X_2 = \sqrt{2^2 (R_1 + R_2)^2}$$

$$Z = \frac{V}{I} = \underline{60} = 0.6 \Omega$$

$$x_1 + x_2 = \sqrt{0.36 - 0.0144} = 0.587 \Omega$$

ANS-10

$$R_1 = 1.15 \Omega, R_2 = 0.0155 \Omega$$

$$\frac{v_1}{v_2} = \frac{200}{250}$$

(a) $\eta = \frac{V_2}{V_1} = \frac{25}{200} = \frac{1}{8}$

$$R'_1 = n^2 R_1 = \frac{1}{64} \times 0.0155 \times 10 = 0.0179$$

$$R_{\text{net}} = 0.0155 + 0.0179 = 0.0334 \Omega$$

(b) Total drop on full load $= I_1 R_1 + I_2 R_2$.

$$I_1 = \frac{40 \times 10^3}{2000} = 20 \text{ A}$$

$$I_2 = \frac{40 \times 10^3}{250} = 160 \text{ A}$$

$$\therefore \text{Total drop} = 20 \times 1.15 + 160 \times 0.0155 \\ = 25.48 \text{ V}$$

(c) $P_c = I_1^2 R_1 + I_2^2 R_2$

$$= (20)^2 \times 1.15 + (160)^2 \times 0.0155$$

$$= 460 + 396.8 = 856.8 \text{ W}$$

ANS-11

$$n=6$$

$$V = 50 \text{ Hz}$$

$$R_1 = 0.9$$

$$R_2 = 0.3$$

$$X_1 = 5$$

$$X_2 = 0.13$$

(a) $I = 200 \text{ A}$,

$$P_c = I^2 (R_1 + R_2) = (200)^2 (1.2) = 48 \text{ kW}$$

$$P = V I$$

$$V = \frac{48 \times 10^3}{200} = 240 \text{ V}$$

$$Z = \sqrt{(R_1 + R_2)^2 + (X_1 + X_2)^2}$$

$$= \sqrt{(1.2)^2 + (5.13)^2} = \sqrt{1.44 + 26.3} \\ = 5.26 \Omega$$

$$V = I Z = 200 \times 5.26 = 1052 \text{ V}$$

$$\tan \theta = \frac{R_1 + R_2}{X_1 + X_2} = \frac{1.2}{5.13} = 0.234$$

$$\phi = \tan^{-1} 0.234 = 13.17^\circ$$

$$\text{Power factor} = \cos \phi = \cos (13.17^\circ) = 0.97$$

Ans-12

ohmic loss = 1% of output.

$$\frac{IR}{V} = \frac{1}{100} = 0.01$$

Resistance drop = 5% of voltage.

$$I_x = \frac{5}{100} V$$

$$\frac{Ix}{V} = 0.05$$

$$\text{Regulation} = \frac{IR \cos \theta}{V} \pm \frac{E \sin \theta}{V}$$

(a)

0.8 lag

$$\therefore \% \text{ regulation} = (0.01)(0.8) + (0.05) = 3.8\%$$

(b)

unity

$$\sin \theta = 0 \text{ (as } \theta = 0)$$

$$\therefore \% \text{ regulation} = \frac{IR}{V} (1) = 1\%$$

(c)

0.8 lead

$$\therefore \% \text{ regulation} = \left(\frac{IR \cos \theta}{V} - \frac{I \sin \theta}{V} \right) \times 100$$

$$= (0.01)(0.8) - (0.05)(0.6)$$

$$= 2.29\%$$

ANS-13

$$P_c = 436 \text{ W}, I = 10 \text{ A}, V = 100 \text{ V}$$

$$\text{P.f.} = 0.8(+)$$

$$R_1 + R_2 = \frac{P_c}{I^2} = \frac{436}{100} = 4.36 \Omega$$

$$Z = \frac{V}{I} = 10 \Omega, X = \sqrt{Z^2 - (R_1 + R_2)^2} = 9 \Omega$$

$$n = \frac{E_2}{E_1} = \frac{6600}{330} = 20$$

$$\frac{V_2}{V_1} = 20$$

$$V_2 = 20 \times 330 = 6600 \text{ V}$$

$$\text{Regulation} = IR \cos \theta + IX \sin \theta$$

$$I = \frac{100 \times 10^3}{6600} = 15.15 \text{ A}$$

$$\therefore \text{Regulation} = 15.15 (4.36 \times 0.8 + 9 \times 0.6) \\ = 134 \text{ V}$$

$$\therefore V_2' = V_2 + 134 \\ = 6600 + 134 = 6734 \text{ V}$$

ANS-15

$$P_c = 1600 \text{ W} \text{ at full load}$$

$$P_i = 1400 \text{ W}$$

a) Pf = 1

$$\eta = \frac{X \sqrt{I} \cos \theta}{\sqrt{V} \sqrt{I} \cos \theta + P_i + P_c}, \cos \theta = 1$$

$$\eta = \frac{\pi VI}{\pi VT + P_i + P_c}$$

At 25% load output = $\frac{VI}{4} = \frac{150}{4} = 37.5 \text{ kW}$

$$P_c = \frac{P_i}{\pi^2} = \frac{1400}{16} = 87.5 \text{ W}$$

$$\eta = \frac{37.5 \times 10^3 \times 100}{37.5 \times 10^3 + 1400 + 87.5} = 96.18\%$$

At 33% load output = $1500 \times \frac{33}{100} = 49.5 \text{ kW}$

$$P_c = \frac{1400}{(3.03)^2} = 152.5 \text{ W}$$

$$\eta = \frac{49500 \times 100}{49500 + 152.5 + 1400} = 97\%$$

At full load

$$\eta = \frac{150 \times 10^3 \times 100}{150 \times 10^3 + 1400 + 1600} = 98\%$$

(b) $\cos \theta = 0.8 \text{ lag}$

At 25% load, output = $150 \times 0.8 \times \frac{1}{4} = 30 \text{ kW}$

$$\eta = \frac{30 \times 10^3 \times 100}{30 \times 10^3 + 1400 + 1400} = \frac{30 \times 10^3 \times 100}{30 \times 10^3 + 1400 + 87.5}$$

$$\eta = \frac{30 \times 10^3}{31487.5} \times 100 = 95.27\%$$

At 33% load output = $49.5 \times 0.8 = 39.6 \text{ kW}$

$$\begin{aligned}\eta &= \frac{39.6 \times 10^3}{39.6 \times 10^3 + 1400 + 152.5} \times 100 \\ &= 96.22\%\end{aligned}$$

At full load

$$\eta = \frac{150 \times 0.8 \times 10^3}{150 \times 0.8 \times 10^3 + 1400 + 1600} \times 100$$

$$= 97.50\%$$

Ans-16

$$P_i = 350 \text{ W}, P_c = 400 \text{ W}$$

$$\eta = \frac{V_i}{V_i + P_i + P_c} \quad [\cos \theta = 1]$$

$$(a) \text{ full load } \eta = \frac{25 \times 10^3}{25 \times 10^3 + 350 + 400} \times 100 = 97.08\%$$

$$(b) \text{ half load } \eta = \frac{25 \times 10^3 \times 0.5}{25 \times 10^3 \times 0.5 + 350 + 87.5} \times 100 = 96.0\%$$

$$\left(P_c = \frac{P_i}{n^2} \right)$$

$$(c) \text{ load } n = \sqrt{\frac{P_i}{P_c}} \times n = \sqrt{\frac{350}{400}} \times 25 \text{ kVA} = 23.4 \text{ kVA}$$

At max efficiency $\eta = \frac{P_i}{P_i + P_c} = 350 \text{ W}$

Ans-17

$$\eta = \frac{VI \cos \theta}{VI \cos \theta + P_i + P_c}$$

$$\eta_{\max} = 0.98 = \frac{15k}{15k + 2x}$$

$$\Rightarrow x = 153 \text{ W}$$

P_i constant = 153 W

P_c depends on loading $= I^2 R$

12 hours $\rightarrow 2 \text{ kW}$ at 0.5 pF

$$KVA = \frac{2}{0.5} = 4.$$

$$P_c = \frac{P_i}{K^2} = 153 \times \left(\frac{4}{15}\right)^2 = 10.88 \text{ W}$$

Next 6 hours $\rightarrow 12 \text{ kW}$ at 0.8 pF

$$KVA = \frac{12}{0.8} = 15$$

$$P_c = 153 \left(\frac{15}{15}\right)^2 = 153 \text{ W.}$$

Next 6 hours $\rightarrow 18 \text{ kW}$ at 0.9 pF

$$KVA = \frac{18}{0.9} \times 1 = 20$$

$$P_c = 153 \times \left(\frac{20}{15}\right)^2 = 272 \text{ W.}$$

$$\% M = \frac{12x_2 + 6x_{12} + 6x_{18}}{10.88 + 12 + 153x_6 + 2 + 2x_6 + 24x_{153}} \times 100$$

$$= 97.5\%$$

ANS-18

$$P_c = 1000 \text{ W}$$

At full load, $P_i = 1000 \text{ W}$

$$\eta = \frac{\sqrt{I} \cos \theta}{\sqrt{I} \cos \theta + P_i + P_c}$$

$$(i) \eta = \frac{kVI}{kVI + P_i + \frac{P_i}{n^2}}$$

At half load

$$P_c = P_i / k^2 = 1000 / 4 = 250 \text{ W}$$

$$\eta = \frac{100 \times 10^3 \times 0.5}{10^5 \times 0.5 + 1000 + 250} = 97.56\%$$

At full load

$$\eta = \frac{10^5}{10^5 + 1000 + 1000} = 98.04\%$$

1.5 load output $P = 100 \times 1.5 = 150 \text{ kVA}$

$$\eta = \frac{150 \times 10^3}{150 \times 10^3 + 1000 + 2250} \times 100 = 97.87\%$$

b) $\cos \theta = 0.8$

half load , $\eta = \frac{50 \times 10^3 \times 0.8}{50 \times 10^3 \times 0.8 + 1000 + 250} \times 100 = 96.96\%$

full load , $\eta = \frac{50 \times 10^3}{10^5 \times 0.8 + 1000 + 1000} \times 100 = 97.56\%$

1.5 load , $\eta = \frac{1.5 \times 10^5 \times 0.8}{1.5 \times 10^5 \times 0.8 + 1000 + 2250} \times 100 = 97.36\%$